
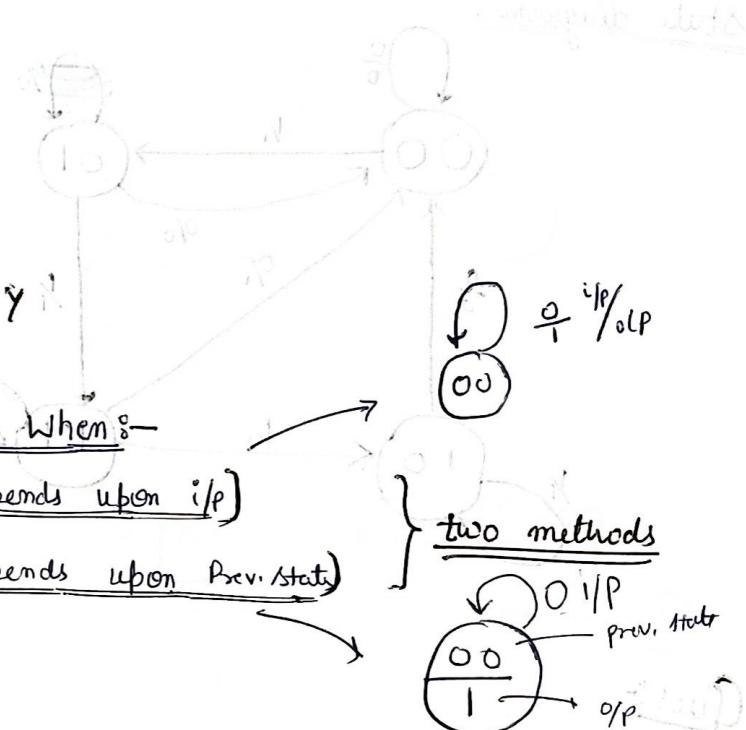
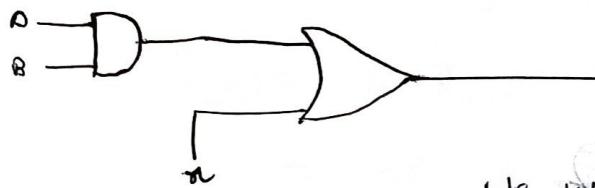
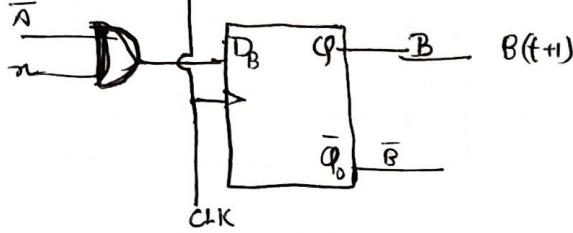

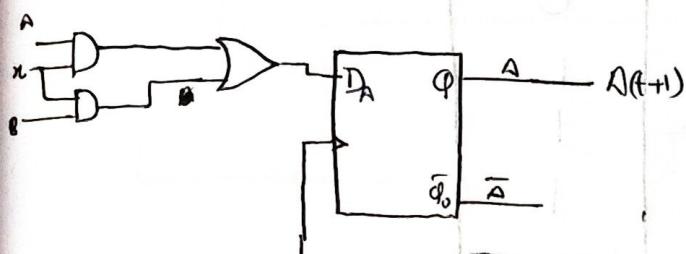
## # Unit-4 [Analysis of Sequential Circuit]

\* In analysis of sequential circuit, circuit or state equation given and we do analysis about various states and output of CKT.

Ques:- Derive the state table & state diagram of synchronous sequential ckt q



We Use When :-

① Melay Method  $\rightarrow$  (output depends upon i/p)

② Moore method  $\rightarrow$  (o/p depends upon prev. state)

} two methods

Ans :- State Equation :-

$$A(t+1) = D_A = A_n + B_n = n(A+B) \quad \text{--- (1)}$$

$$B(t+1) = D_B = \bar{A} * n \Rightarrow \bar{A}n \quad \text{--- (2)}$$


$$Y = AB + n \quad \text{--- (3)}$$

now,

## State table


Prev. state	input	next state		o/p
		A(t+1)	B(t+1)	
0 0	0	0	0	0
0 0	1	0	1	1
0 1	0	0	0	0
0 1	1	1	1	1
1 0	0	0	0	0
1 0	1	1	0	1
1 1	0	0	0	1
1 1	1	1	0	1

## State diagram

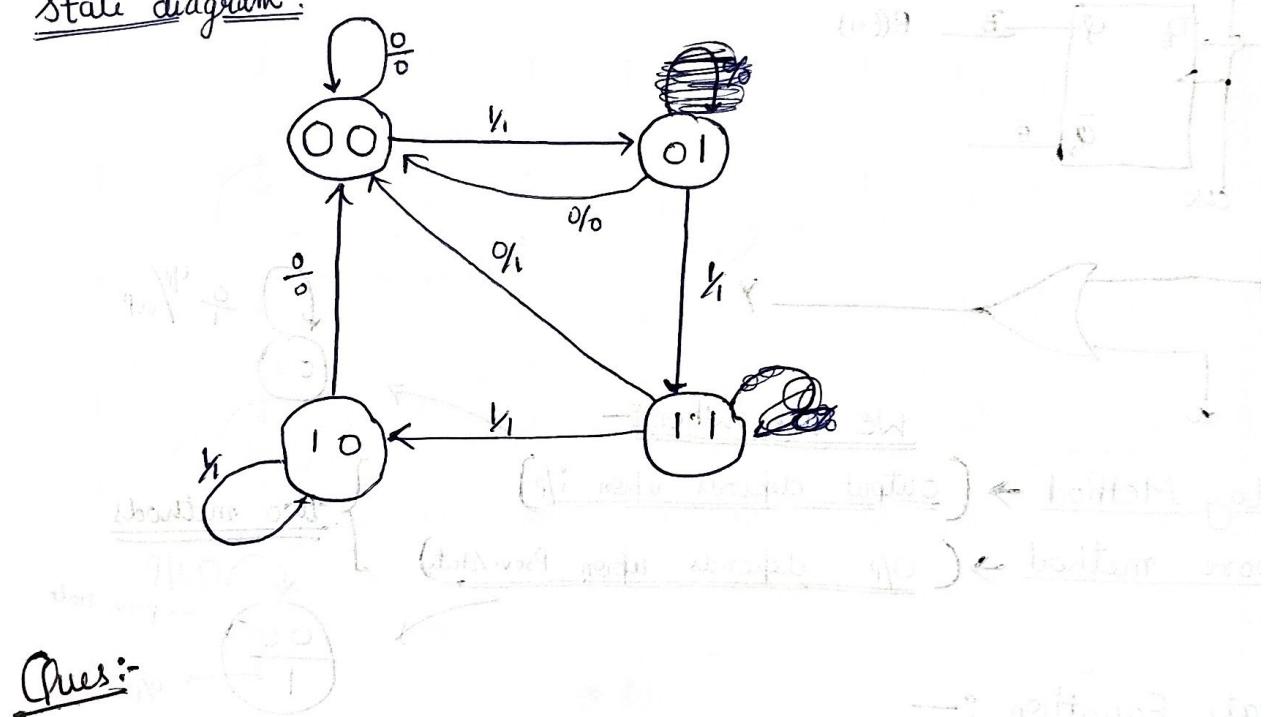

Ques:-

find State table & State diagram of

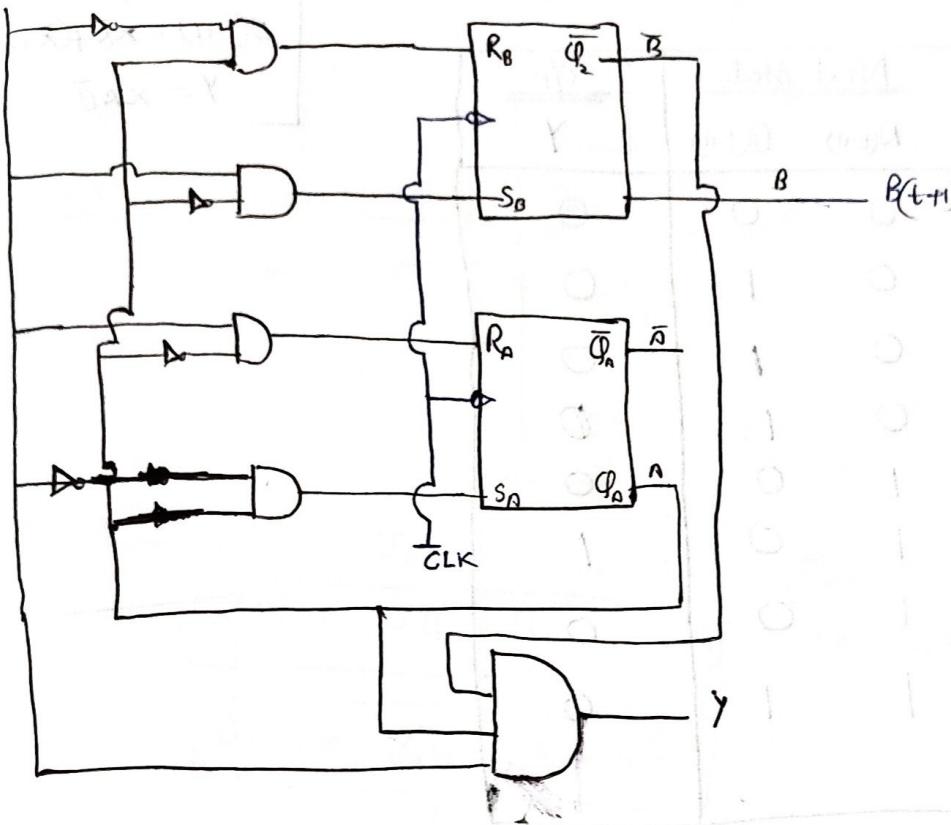

Characteristic eqn of SR F/F

$$Q(t+1) = S + \bar{R}Q$$

$$R_B = A\bar{A}, \quad S_B = \bar{A}\bar{A}$$

$$B(t+1) = S_B + \bar{R}_B \cdot B$$

$$= \bar{A}\bar{A} + (\bar{A} + \bar{n}) \cdot B$$

$$\Rightarrow \bar{A}\bar{A} + \bar{A}B + \bar{n}B$$

$$R_A = \bar{A}\bar{A} \quad S_A = A\bar{A} \quad \Rightarrow \bar{A}B + \bar{A}\bar{A} + \bar{n}B = \boxed{\bar{A}\bar{A} + (\bar{A} + \bar{n})B \Rightarrow B(t+1)}$$

$$A(t+1) = S_A + \bar{R}_A \cdot A$$

$$= \bar{A}A + (\bar{A} + A) \cdot A$$

$$= \bar{A}A + \bar{A}A + A$$

$$\Rightarrow A(1 + \bar{A} + \bar{n})$$

$$\boxed{A(t+1) \Rightarrow A}$$


$$\boxed{Y = \bar{A}AB}$$

## State table.

<u>P.S</u>		<u>i/p</u>	<u>Next State</u>		<u>O/P</u>
A	B	x	A(t+1)	B(t+1)	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	0	0
1	1	1	1	1	0


$$\boxed{\begin{aligned} A(t+1) &= x \\ B(t+1) &= x\bar{A} + (\bar{x} + x)B \\ Y &= xA\bar{B} \end{aligned}}$$

## State diagram

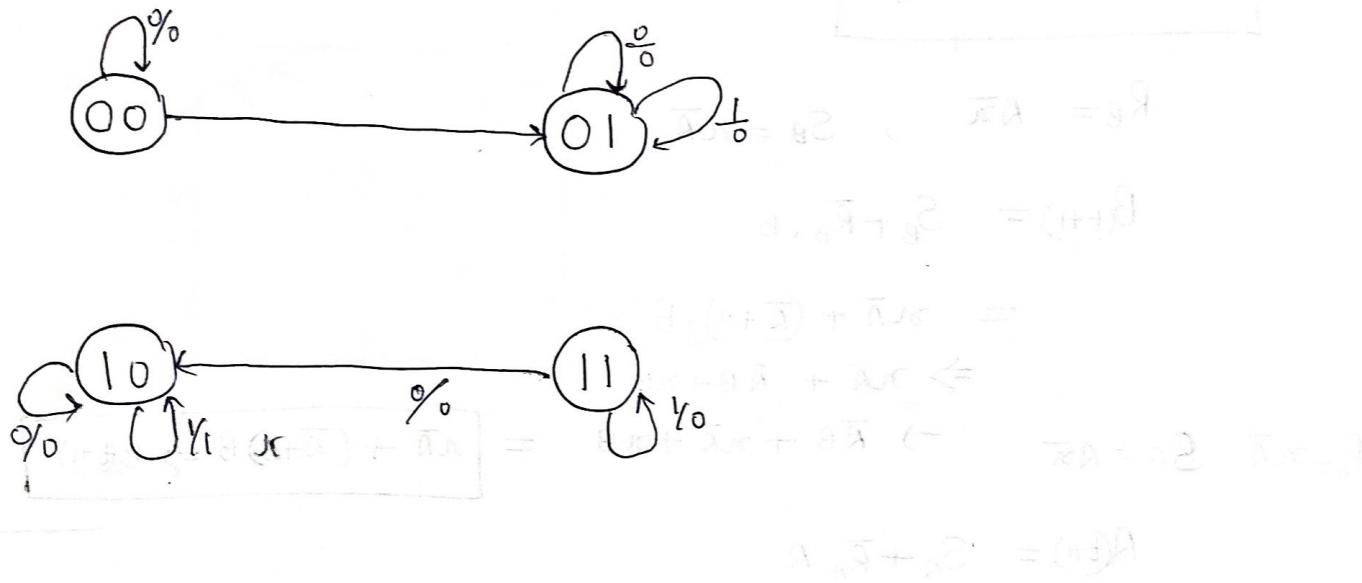

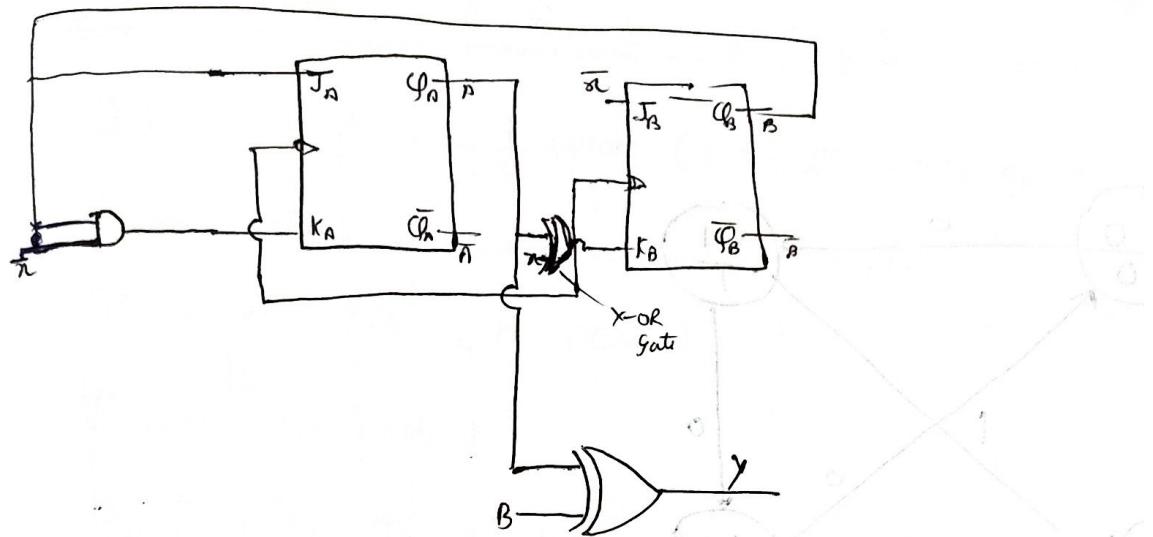Ques:- design the state table & state diagram for the sequential circuit -





State eqn

$$Q_{A(t+1)} = J_A \bar{Q} + K_A Q \quad J_A = B \quad K_A = \bar{x}B \quad \bar{J}_B = \bar{x}$$


$$Q_{B(t+1)} = (A \oplus x) B + \bar{x} \bar{B} \quad K_B = (A \oplus x)$$

$$Y = A \oplus B$$

State table

<u>P.S.</u>		<u><math>x</math></u>	<u>NS</u>		<u><math>y</math></u>
<u><math>A</math></u>	<u><math>B</math></u>	<u><math>x</math></u>	<u><math>A(t+1)</math></u>	<u><math>B(t+1)</math></u>	<u><math>y</math></u>
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	1	1
0	1	1	1	0	1
1	0	0	1	1	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	1	1	0

State diagram

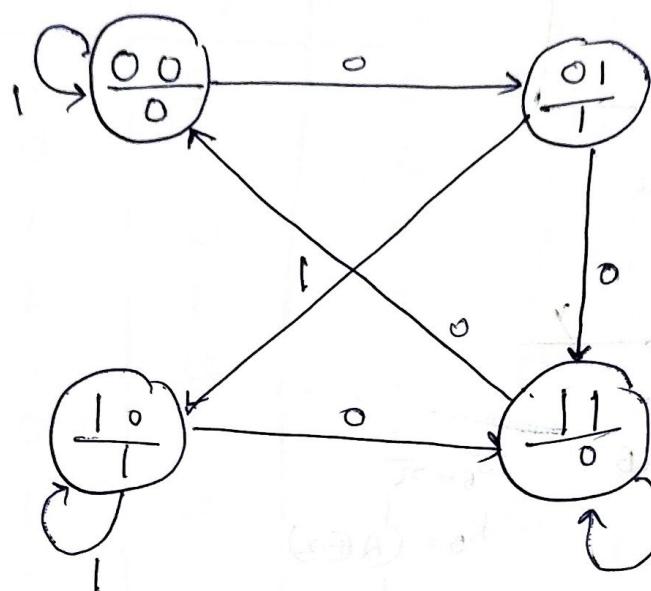


= <sup>stat.</sup>  
Stable    Simplified

P.S	NS		O/P			
A	B	$A(H)$	$B(H)$	$A(H)$	$B(H)$	
0	0	0	1	0	0	01
0	1	1	1	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	00
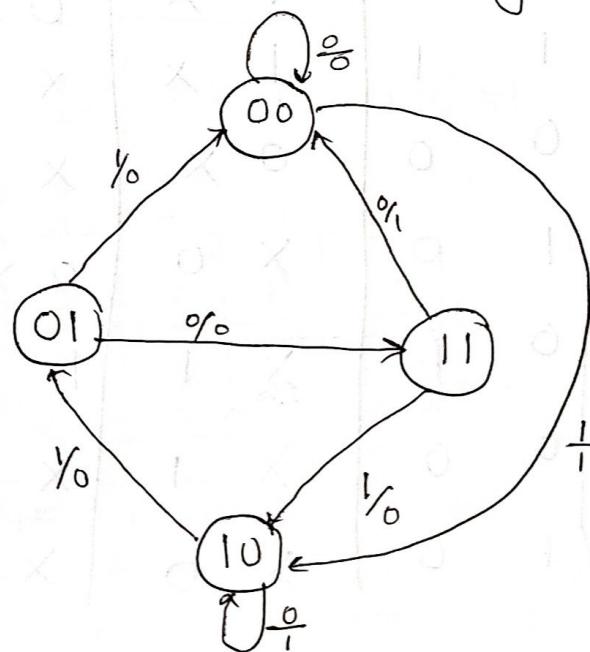
## # Clocked Sequential Synchronous CKt :-

- <1> Determine state diagram (normally given question)
- 2> from state diagram  $\rightarrow$  state table
- 3> State reduction (if possible)
- 4> Binary assignment
- 5> By finding no. of F/F.
- 6> Choose type of F/F (SR, JK, D, T)
- 7> Compare excitation & state table
- 8> By K-map find CKt output.
- 9> Draw logic diagram.

Ques:- A sequential CKt has one ip and one o/p state diagram is shown below design using J-K F/F?



Y-state  
 $2 \oplus 0 \Rightarrow f_1$

Ans:-

Given that

## State table

Q)

Prev. State		I/P		N. S		O/P	
A	B	$\bar{x}$	x	$A(t+1)$	$B(t+1)$	y	
0	0	0	0	0	0	0	
0	0	1	1	1	0	1	
0	1	0	1	1	1	0	
0	1	1	0	0	0	0	
1	0	0	1	0	0	0	
1	0	1	0	1	0	0	
1	1	0	0	0	1	1	
1	1	1	1	1	0	0	

Excitation table ( $J_k$ )

$G(t) \cdot G(t+1)$		$J$	$K$
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

= Compare

P.S.

A		B		I/P		N. S		$J_0, K_0$		$J_1, K_1$		Y	
				$\bar{x}$		$A(t+1) \quad B(t+1)$							
0	0	0	0	0	0	0	0	0	x	0	x	0	0
0	0	0	1	1	0	1	0	1	x	0	x	1	0
0	1	0	0	1	1	1	1	1	x	0	x	1	0
0	1	0	1	0	0	0	0	1	x	0	x	0	0
1	0	0	0	0	1	0	1	0	x	0	x	1	0
1	0	0	1	1	0	0	0	0	x	0	x	0	0
1	1	0	0	0	1	1	1	1	x	1	x	0	0
1	1	0	1	0	0	0	0	1	x	1	x	1	1
1	1	1	0	1	0	1	0	0	x	0	x	1	0
1	1	1	1	1	0	0	0	0	x	1	x	0	0

$$J_0 = \sum_m (1, 2) + \sum_d (4, 5, 6, 7)$$

~~BAZ~~

	00	01	11	10
0		1		1
1	x	x	x	x

$$J_0 = \bar{x} \cdot \text{BAZ} + x \cdot \text{BAZ}$$

$$J_0 = \bar{x} \oplus A(t+1) \quad x \oplus B$$

$$K_0 = \Sigma m(5, 6) + \Sigma d(0, 1, 2, 3)$$

$A$

$B$

	00	01	11	10
0	X	X	X	X
1				

$$K_0 = \pi B \bar{A} \bar{B} + \cancel{\pi A B} \pi B$$

$$K_0 = \pi \oplus B \bar{B}$$

$$J_1 = \Sigma m(5) + \Sigma d(2, 3, 6, 7)$$

$A$

$B$

	00	01	11	10
0	.	.	X	X
1			X	X

$$J_1 = A \pi$$

$$K_1 = \Sigma m(3, 6, 7) + \Sigma d(0, 1, 4, 5)$$

$A$

$B$

	00	01	11	10
0	X	X	1	.
1	X	X	1	1

$$K_1 = A + \pi$$

$$Y = \Sigma m(1, 6) + \Sigma d(0, 2, 3)$$


$A$

$B$


	00	01	11	10
0	.	1	.	.
1			1	1

$$Y \Rightarrow \bar{A} \bar{B} \bar{A} + A B \bar{A}$$

now,  
CKT diagram

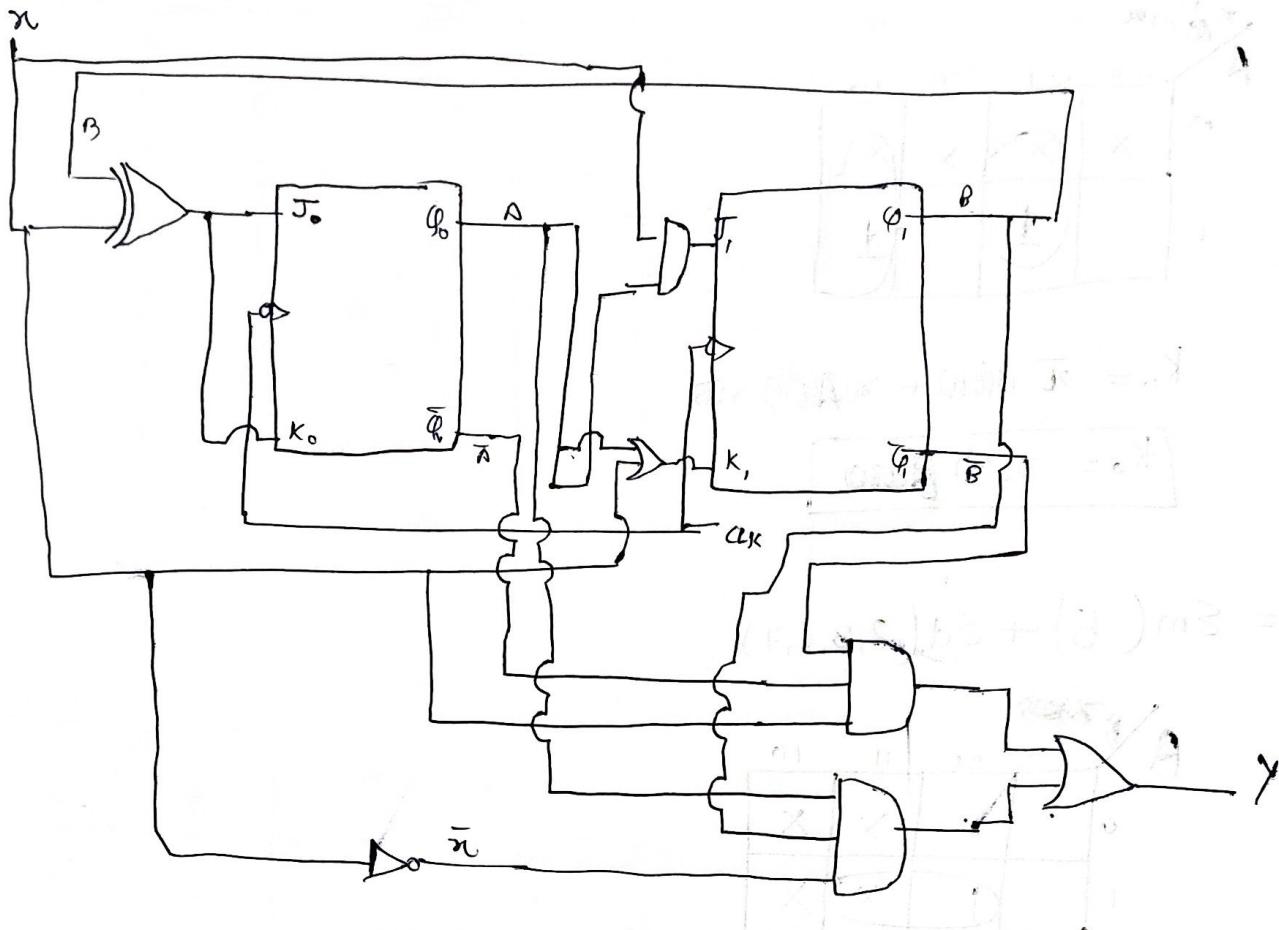

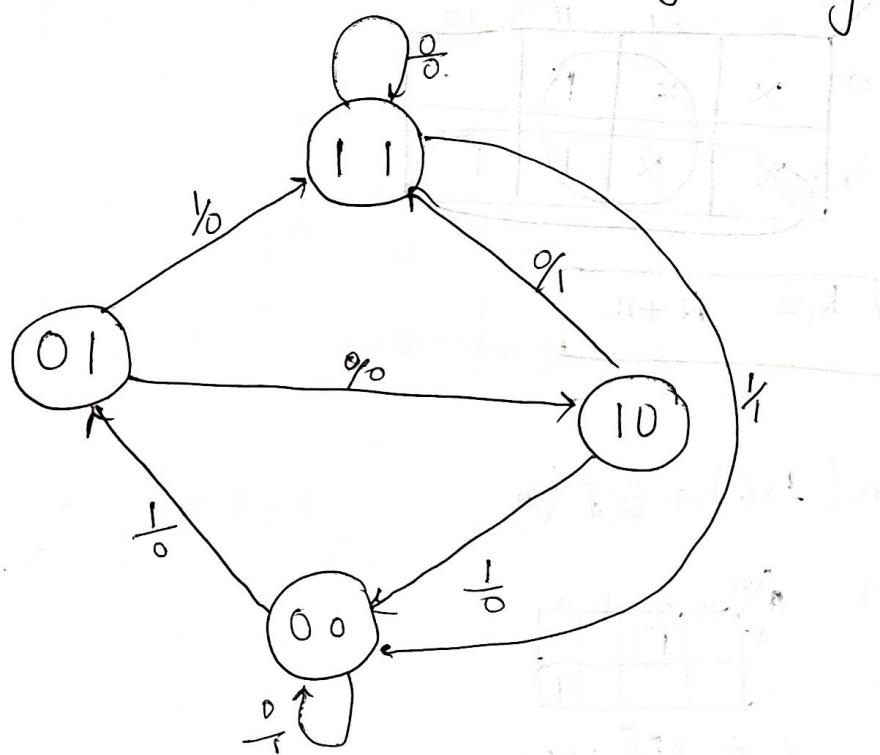Ques:- A sequential diagram is shown below. Design using, J-K F/F q




Ques:- for the state diagram shown in fig. design the ckt

Using -

(a) T F/F

(b) S-R F/F

(c) J-K F/F

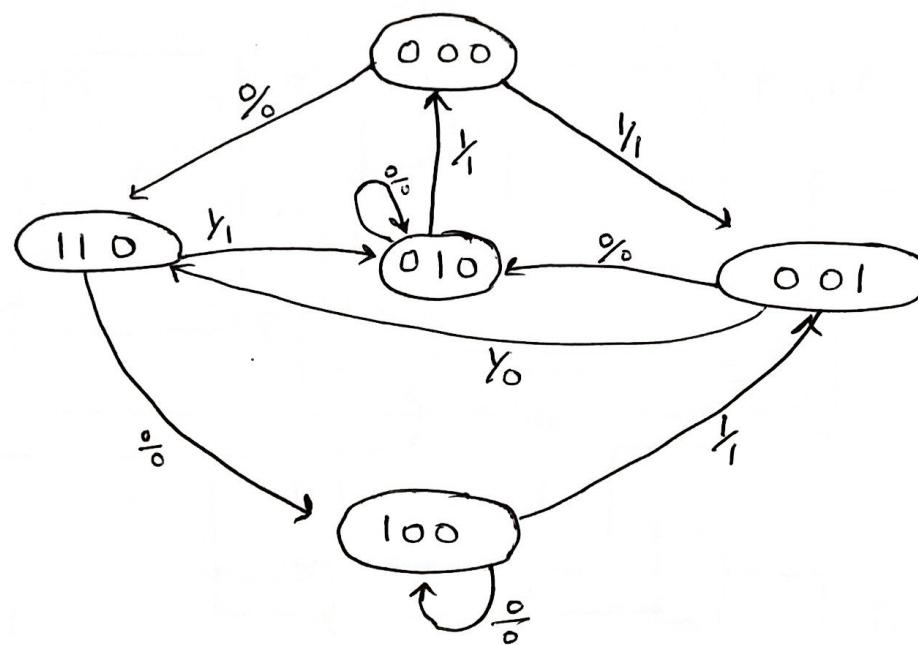

Sol:

(a)

State table

Prev. State			i/p	Next state			O/P
A	B	C	x	A(t+1)	B(t+1)	C(t+1)	y
0	0	0	0	1	1	0	0
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	0
0	0	1	1	1	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	0	0	1	1
1	1	0	0	0	1	0	0
1	1	0	1	0	1	0	1
0	1	0	1	0	0	0	1
0	1	0	0	0	1	0	0

Excitation table of T-F/F

$\Phi(t)$	$\Phi_{(t+1)}$	T
0	0	0
0	1	1
1	0	1
1	1	0

Tham

A	B	C	x	A <sub>(t+1)</sub>	B <sub>(t+1)</sub>	C <sub>(t+1)</sub>	T <sub>A</sub>	T <sub>B</sub>	T <sub>C</sub>	y
0	0	0	0	1	1	0	1	1	0	0
0	0	0	1	0	0	1	0	1	1	1
0	0	1	0	0	1	0	0	1	1	0
0	0	1	1	1	1	0	1	1	1	0
1	0	0	0	1	0	0	0	0	0	0
1	0	0	1	0	0	1	1	0	1	1
1	1	0	0	1	0	0	0	1	0	0
1	1	0	1	0	1	0	1	0	0	1
0	1	0	1	0	0	0	0	1	0	1
0	1	0	0	0	1	0	0	0	0	0

$$T_A = \Sigma m(0, 3, 9, 13)$$

$$T_B = \Sigma m(0, 2, 3, 5, 12)$$

$$T_C = \Sigma m(1, 2, 3, 9)$$

$$y = \Sigma m(1, 5, 9, 13)$$



K-Map

for  $T_A$  -

AB \ Cx	00	01	11	10
$\bar{A}\bar{B}$	1		1	
$\bar{A}B$				
AB		1		
$A\bar{B}$		1		

← minterm 5

$$T_A = \bar{A}\bar{B}\bar{C}x + \bar{A}\bar{B}Cx + A\bar{C}x$$

for  $T_B$ .

AB	Cx	00	01	11	10
00	0	1	1	1	1
01	1	0	0	0	0
11	1	0	0	0	0
10	0	1	0	0	0

$$T_B = \bar{A}\bar{B}\bar{x} + AB\bar{C}\bar{x} + \bar{A}B\bar{C}x + \bar{A}\bar{B}C$$

for the  $T_C$

AB	Cx	00	01	11	10
00	1	1	1	1	1
01	0	1	0	0	0
11	0	1	0	0	0
10	0	1	0	0	0

$$T_C = \bar{B}\bar{C}x + \bar{A}\bar{B}C$$

for  $Y$

AB	Cx	00	01	11	10
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$$(0,1,0,0)_{m3} = T$$


$$(1,0,1,0)_{m3} = \bar{T}$$

$$Y = \bar{C}x$$


$$(0,0,1,1)_{m3} = Y$$

$$= AT \times \bar{C}$$

Ckt diagram  $\rightarrow$

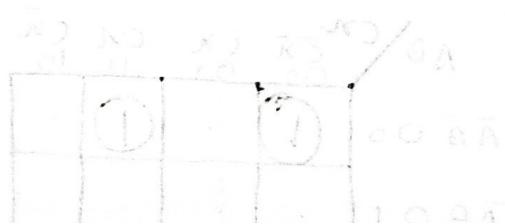

## Ckt diagram

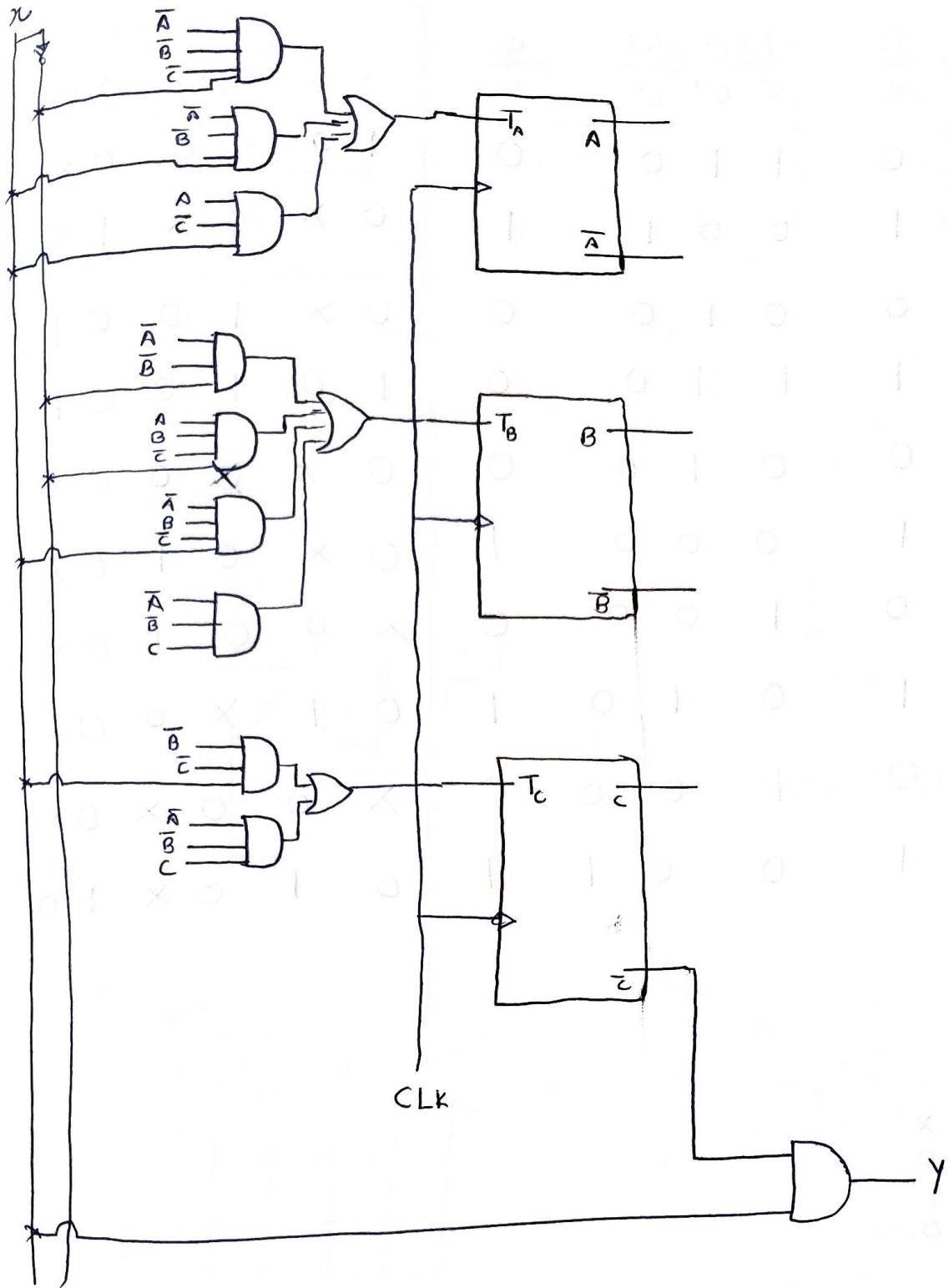

Using S-R

state table


Table - 2

Table - 2

Prev. State A B C	i/p x	Next state A <sup>+</sup> B <sup>+</sup> C <sup>+</sup>			o/p y	S <sub>A</sub> R <sub>A</sub>	S <sub>B</sub> R <sub>B</sub>	S <sub>C</sub> R <sub>C</sub>
		A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>				
0 0 0	0	1	1	0	0	1 0	1 0	0 X
0 0 0	1	0	0	1	1	0 X	0 X	1 0
0 0 1	0	0	1	0	0	0 X	1 0	0 1
0 0 1	1	1	1	0	0	1 0	1 0	0 1
0 1 0	0	0	1	0	0	0 X	X 0	0 0 X
0 1 0	1	0	0	0	1	0 X	0 1	0 X
1 1 0	0	1	0	0	0	X 0	0 1	0 X
1 1 0	1	0	1	0	1	0 1	X 0	0 0 X
1 0 0	0	1	0	0	0	X 0	0 X	0 X
1 0 0	1	0	0	1	1	0 1	0 X	1 0

Characteristics of S-R

S <sub>t</sub>	C <sub>t+1</sub>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

 

min terms —

$$S_A = \sum m(0, 3) + \sum d(12, 8)$$

$$R_A = \sum m(0, 13, 9) + \sum d(1, 2, 4, 5)$$


$$Y = \sum m(1, 5, 13, 9)$$

$$S_B = \sum m(0, 2, 3) + \sum d(4, 13)$$




$$R_B = \sum m(5, 12) + \sum d(1, 6, 9)$$

$$S_C = \sum m(1, 9)$$
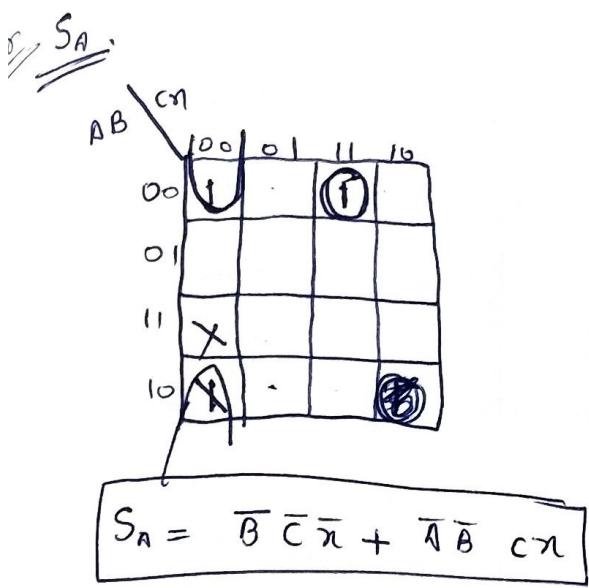
$$R_C = \sum m(2, 3) + \sum d(0, 4, 5, 8, 12, 13)$$





$$R_A = \overline{C} \bar{n}$$

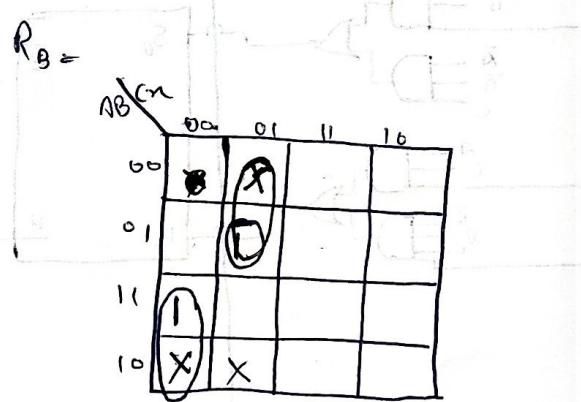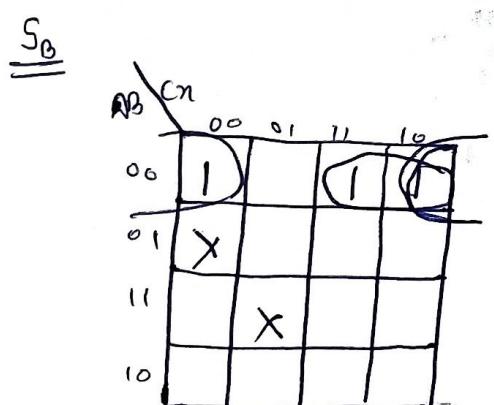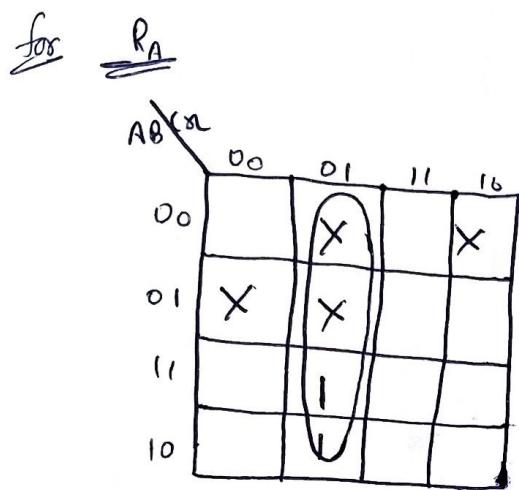

$$S_B = \overline{A} \overline{B} \bar{n} + \overline{A} \overline{B} C$$
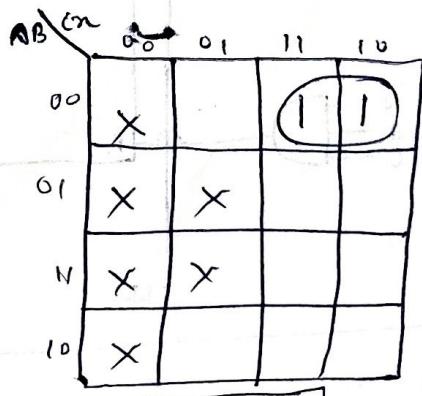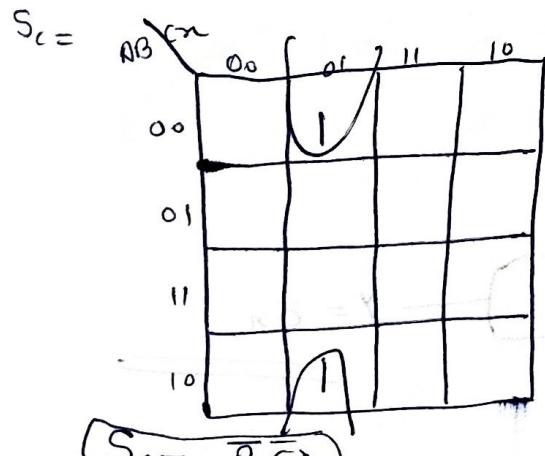
$$R_B = A \overline{C} \bar{n} + \overline{A} B \overline{C} \bar{n}$$




$$R_C = \overline{A} \overline{B} C$$

$y =$

$A \oplus B$	00	01	11	10
00	.			
01		*		
11			*	
10				*

$$Y = \bar{C}n$$

CKT diagram

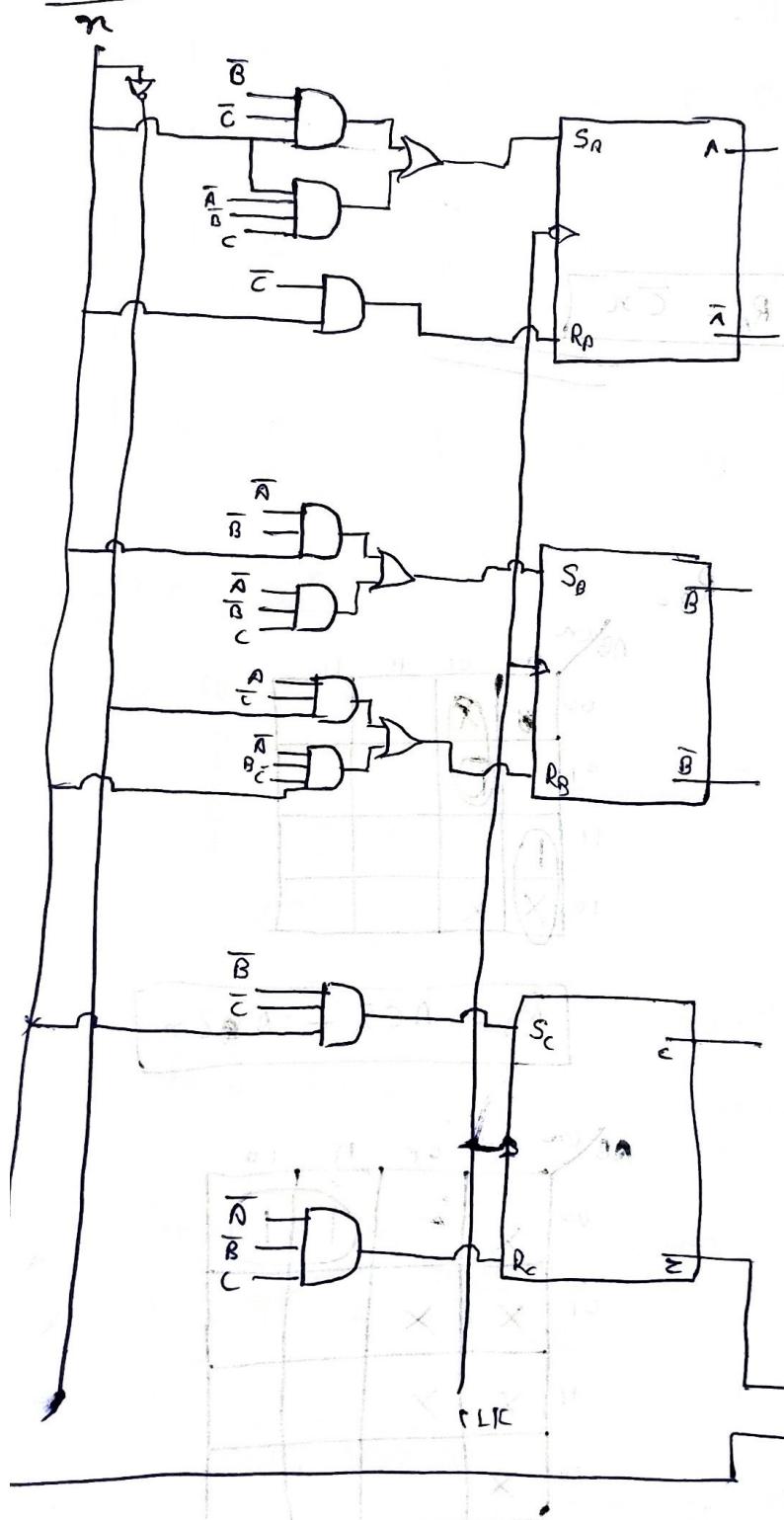

By J-K F/F.

J = excitation table

Q <sub>t+1</sub>		J K	
Q <sub>t+1</sub>	Q <sub>t+1</sub>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

State table

Prev. state	I/P	Next state			O/P	J <sub>A</sub> K <sub>A</sub>	J <sub>B</sub> , K <sub>B</sub>	J <sub>C</sub>
		A <sup>t</sup>	B <sup>t</sup>	C <sup>t</sup>				
0 0 0	0	1	1	0	0	1 X	1 X	0 X
0 0 0	1	0	0	1	1	0 X	0 X	1 X
0 0 1	0	0	1	0	0	0 X	1 X	X 1
0 0 1	1	1	1	0	0	1 X	1 X	X 1
0 1 0	0	0	1	0	0	0 X	X 0	0 X
0 1 0	1	0	0	0	1	0 X	X 1	0 X
1 1 0	0	1	0	0	0	X 0	X 1	0 X
1 1 0	1	0	1	0	1	X 1	X 0	0 X
1 0 0	0	1	0	0	0	X 0	0 X	0 X
1 0 0	1	0	0	1	1	X 1	0 X	1 X

$$J_A = \sum m(0, 3) + \sum d(12, 13, 8, 9)$$

$$K_A = \sum m(9, 13) + \sum d(0, 1, 2, 3, 4, 5)$$

$$J_B = \sum m(0, 2, 3) + \sum d(4, 5, 12, 13)$$

$$K_B = \sum m(5, 12) + \sum d(0, 1, 2, 3, 6, 9)$$

$$J_C = \sum m(1, 9) + \sum d(2, 3)$$

$$K_C = \sum m(2, 3) + \sum d(0, 1, 4, 5, 12, 13, 8, 9)$$

$$Y = \sum m(1, 5, 9, 13)$$

now,

K-map for —

$J_A$ .

$AB \backslash Cn$	00	01	11	10
00	1			
01				
11	X	X		
10		X		

$$J_A = \bar{B}\bar{C}n + \bar{A}\bar{B}Cn$$

$K_A$

$AB \backslash Cn$	00	01	11	10
00	X		X	X
01	X	X		
11			1	
10			1	

$$K_A = \bar{C}n$$

$J_B$

$AB \backslash Cn$	00	01	11	10
00	1			
01		X		
11	X	X		
10				

$$J_B = \bar{A}\bar{B}\bar{n} + \bar{A}\bar{B}C$$

$K_B$

$AB \backslash Cn$	00	01	11	10
00	X	(X)	X	X
01		1		
11	(1)			
10	X			

$$K_B = \bar{A}\bar{C}n + A\bar{C}\bar{n}$$

$J_C$

$AB \backslash Cn$	00	01	11	10
00		1	X	X
01				
11				
10		1		

$$J_C = \bar{B}\bar{C}n$$

$K_C$

$AB \backslash Cn$	00	01	11	10
00	X	X	1	1
01	X	X		
11	X	X		
10	X	X		


$$K_C = \bar{A}\bar{B}$$

$Y$

$AB \backslash Cn$	00	01	11	10
00		1		
01		1		
11		1		
10		1		

$$Y = \bar{C}n$$

Ckt diagram

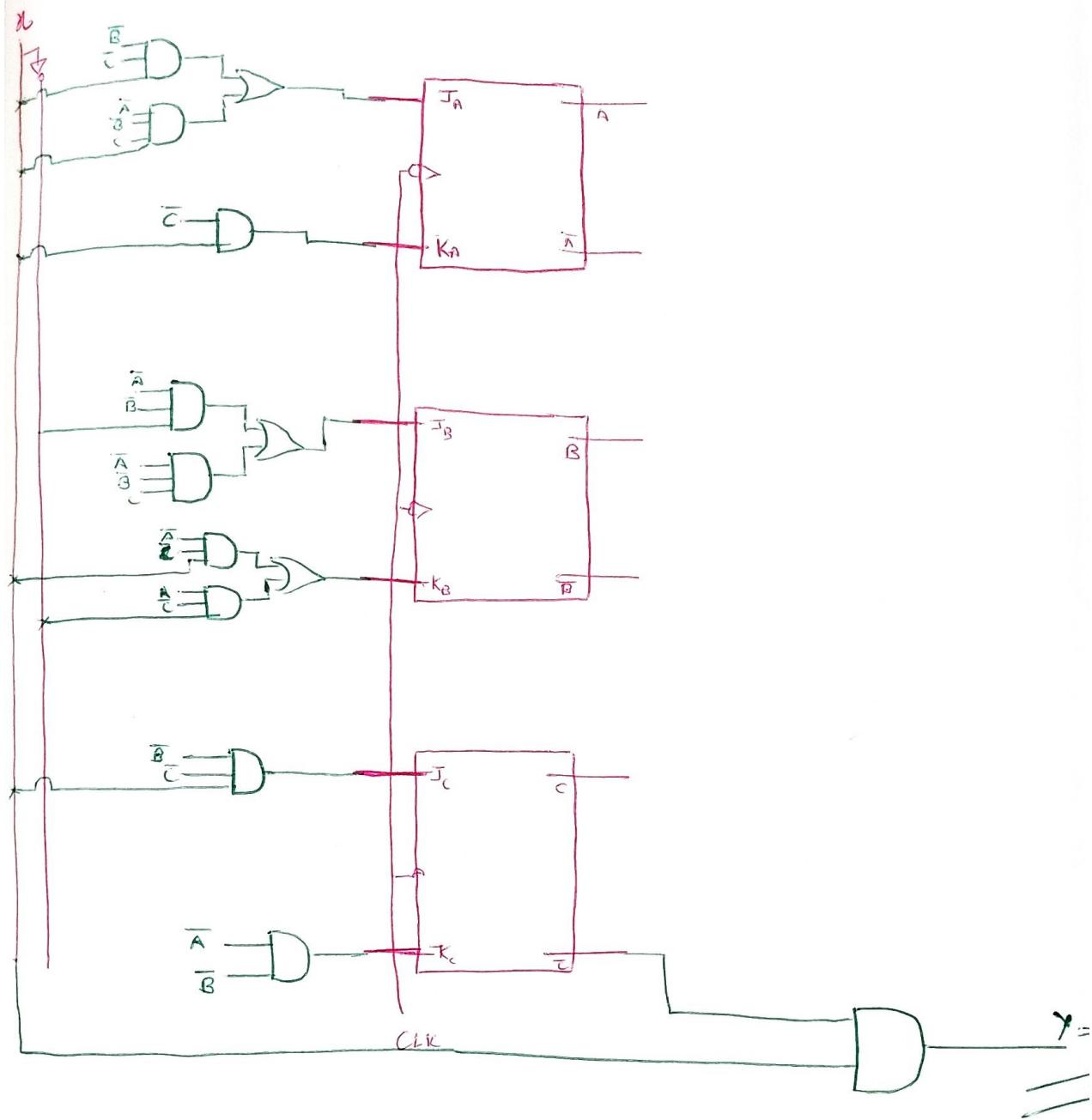

# Analysis of Asynchronous sequential circuit

- Steps :-
- 1) determine the next secondary state & output equations from given sequential ckt.
  - 2) construct the state table
  - 3) construct transition table
  - 4) construct the output map.


Pues :- An Asynchronous Sequential ckt is design by the following excitation output  $f^n$  -

$$y^+ = x_1 x_2 + (x_1 + x_2) y$$

$$z = y^+$$

- (i) Draw logic diagram of ckt?
- (ii) Derive transition table & output map?

Ans. (i)

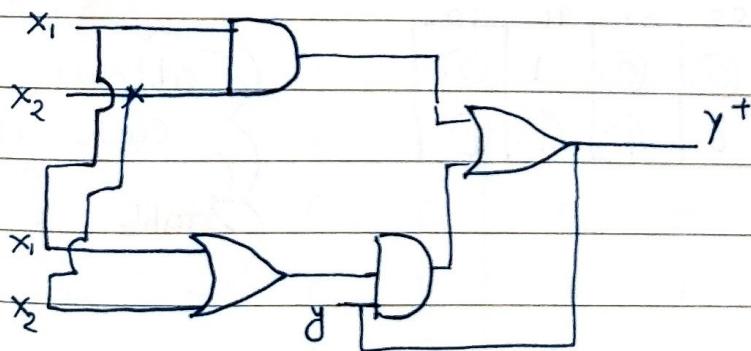

(ii) now,

We construct the ~~ex~~ state table first -

Prev. state = Y

N.S =  $y^+$

i/p =  $x_1, x_2$

O/p = z

= State table

<u>Prev. S.</u>	<u>i/p</u>	<u>N.S</u>	<u>O/p</u>
<u>y</u>	<u>x<sub>1</sub> x<sub>2</sub></u>	<u>y<sup>+</sup></u>	<u>z</u>
0	0 0	0	0
0	0 1	0	0
0	1 0	0	0
0	1 1	1	1
1	0 0	0	0
1	0 1	1	1
1	1 0	1	1
1	1 1	1	1

= transition table

<u>y</u>	<u>x<sub>1</sub> x<sub>2</sub></u>	<u>x<sub>1</sub> x<sub>2</sub> (i/p)</u>			
<u>y</u>	<u>(P.S)</u>	<u>00</u>	<u>01</u>	<u>11</u>	<u>10</u>
0	0	0	0	1	0
1	0	0	1	1	1

(atleast one circle in each column)

stable  $(Y_i = Y_i^+)$

= Output mapping -

<u>y</u>	<u>x<sub>1</sub> x<sub>2</sub></u>	<u>00</u>	<u>01</u>	<u>11</u>	<u>10</u>
<u>y</u>	<u>(P.S)</u>	<u>0</u>	<u>-</u>	<u>-</u>	<u>0</u>
0	0	0	0	-	0
1	0	-	1	1	1

Ques :- An asynchronous sequential ckt has two internal states & one o/p. The excitation and o/p function describing the ckt as follows -

$$Y_1 = X_1 X_2 + X_1 Y_2 + X_2 y_1$$

$$Y_2 = X_2 + x_1 y_1 y_2 + x_1 y_1$$

$$z = x_2 + y_1$$

## State table —

<u>Prev. stat.</u>	<u>i/p</u>	<u>N. S</u>	<u>O/p</u>			
$y_1$	$y_2$	$x_1$	$x_2$	$y_1$	$y_2$	$z$
0	0	0	0	0	0	0
0	0	0	1	0	1	1
0	0	1	0	0	0	0
0	0	1	1	1	1	1
0	1	0	0	0	0	0
0	1	0	1	0	1	1
0	1	1	0	1	0	0
0	1	1	1	1	1	1
1	0	0	0	0	0	1
1	0	0	1	1	1	1
1	0	1	0	0	1	1
1	0	1	1	1	1	1
1	1	0	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

transition table

$y_1, y_2 \backslash x_1 x_2$	00	01	11	10
00	00	01	11	00
01	00	01	11	10
11	00	11	11	1
10	00	11	11	01

Output mapping

$y_1, y_2 \backslash x_1 x_2$	00	01	11	10
00	0	-	-	0
01	-	1	-	-
11	-	1	1	1
10	-	-	-	-


Ques. Draw the logic diagram and check stability of following expression -

$$Y_1 = \bar{x} \bar{y}_2$$

$$Y_2 = \bar{x} \bar{y}_1$$

$$Z = \bar{x} y_1$$

Ans:-

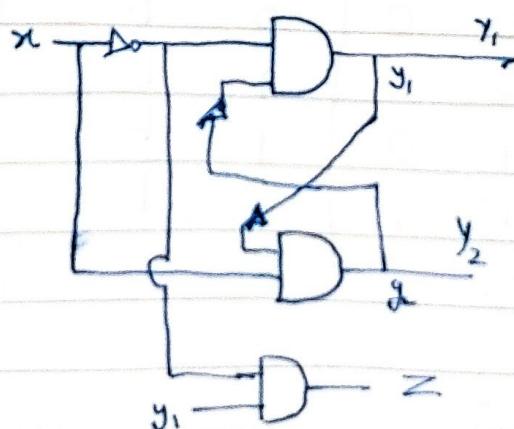

State table

P.S	i/p	Next. State	o/p
$y_1\ y_2$	X	$y_1\ y_2$	Z
0 0	0	1 0	0
0 0	1	0 1	0
0 1	0	0 0	0
0 1	1	0 1	0
1 0	0	1 0	1
1 0	1	0 0	0
1 1	0	0 0	1
1 1	1	0 0	0

transition table

<del><math>y_1\ y_2</math></del>	00	01	11	10
0				
1				


<del><math>y_1\ y_2</math></del>	<del>X</del>	0	1
00	10	01	
01	00	01	
11	00	00	
10	10	00	

gt is stable

Output mapping

<del><math>y_1\ y_2</math></del>	0	1
00	-	-
01	-	0
11	-	-
10	1	-

\* Ques:- find the flow table and transition table using S-R latch.

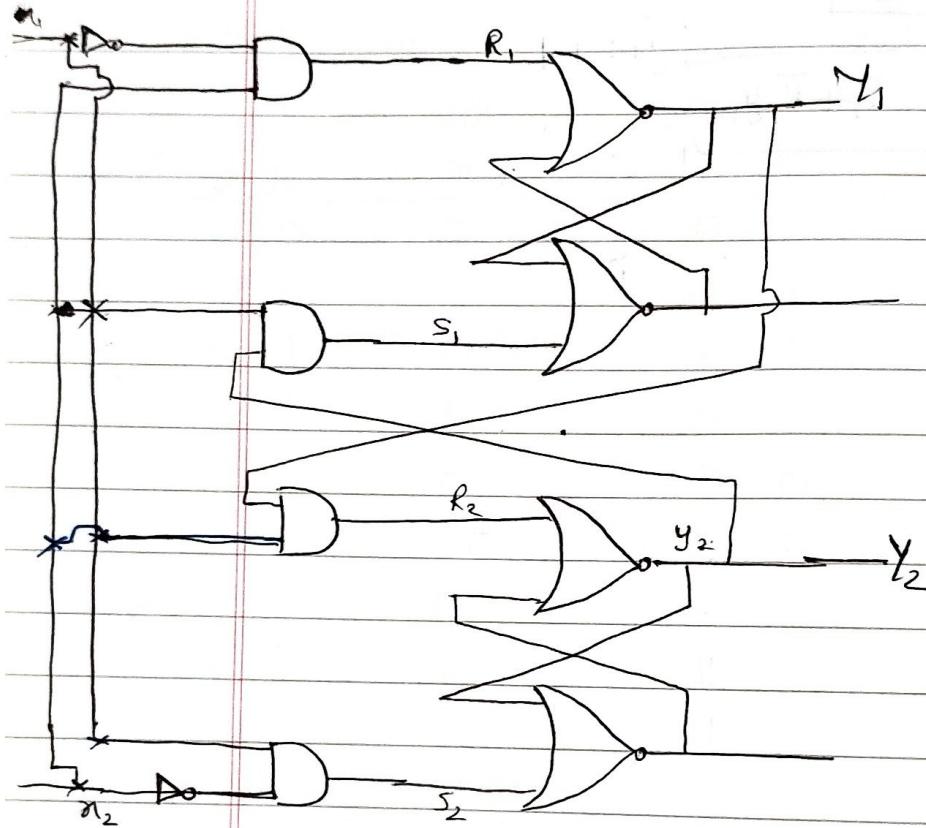Ans.

Characteristic Eqn of SR latch

$$Y = S + \bar{R}Y$$

$$Y_1 = S_1 + \bar{R}_1 Y_1$$

$$Y_2 = S_2 + \bar{R}_2 Y_2$$

$$S_1 = \pi_1 y_2, \quad R_1 = \pi_1 \pi_2$$

$$Y_1 = \pi_1 y_2 + (\pi_1 \pi_2) y_1$$

$$\Rightarrow Y_1 = \pi_1 y_2 + \pi_1 y_1 + \bar{\pi}_2 y_1$$

$$Y_2 = S_2 + R_2 y_2$$

$$S_2 = x_1 \bar{x}_2, \quad R_2 = x_2 y_1.$$

$$Y_2 = x_1 \bar{x}_2 + (\bar{x}_2 y_1) y_2.$$

$$Y_2 = x_1 \bar{x}_2 + (\bar{x}_2 + \bar{y}_1) y_2$$

$$Y_2 = x_1 \bar{x}_2 + \bar{x}_2 y_2 + \bar{y}_1 y_2$$

= State table

<u>Prev. State</u>	<u>i/p</u>	<u>N.S.</u>
<u><math>x_1 x_2</math></u>	<u><math>x_1 x_2</math></u>	<u><math>y_1 y_2</math></u>

0 0	0 0	0 0
-----	-----	-----

0 0	0 1	0 0
-----	-----	-----

0 0	1 0	0 1
-----	-----	-----

0 0	1 1	0 0
-----	-----	-----

0 1	0 0	0 1
-----	-----	-----

0 1	0 1	0 1
-----	-----	-----

0 1	1 0	1 1
-----	-----	-----

0 1	1 1	1 1
-----	-----	-----

1 0	0 0	1 0
-----	-----	-----

1 0	0 1	0 0
-----	-----	-----

1 0	1 0	1 1
-----	-----	-----

1 0	1 1	1 0
-----	-----	-----

1 1	0 0	0 1
-----	-----	-----

1 1	0 1	0 0
-----	-----	-----

1 1	1 0	1 1
-----	-----	-----

1 1	1 1	1 0
-----	-----	-----

» transition table

$y_1, y_2$	00	01	11	10
00	00	00	00	01
01	01	01	11	11
11	11	00	10	11
10	10	00	10	11

= stable

reverse Engineering

$y_1, y_2$	00	01	11	10
00	1	0	1	1
01	1	0	0	0
11	1	0	0	0
10	0	0	0	0

for  $y_2$

for  $y_1$

$y_1, y_2$	00	01	11	10
00	0	0	0	1
01	1	1	1	1
11	1	0	0	1
10	0	0	0	1


= now, flow table →

let  $\begin{cases} 00 = a \\ 01 = b \\ 11 = c \\ 10 = d \end{cases}$

P.S.  $\Rightarrow$

	$x_1 x_2$	$y_1 y_2$	00	01	11	10
a	(a)	(a)	(a)	b		
b	(b)	(b)	c	c		
c	(c)	a	d	(c)		
d	(d)	a	(d)	c		

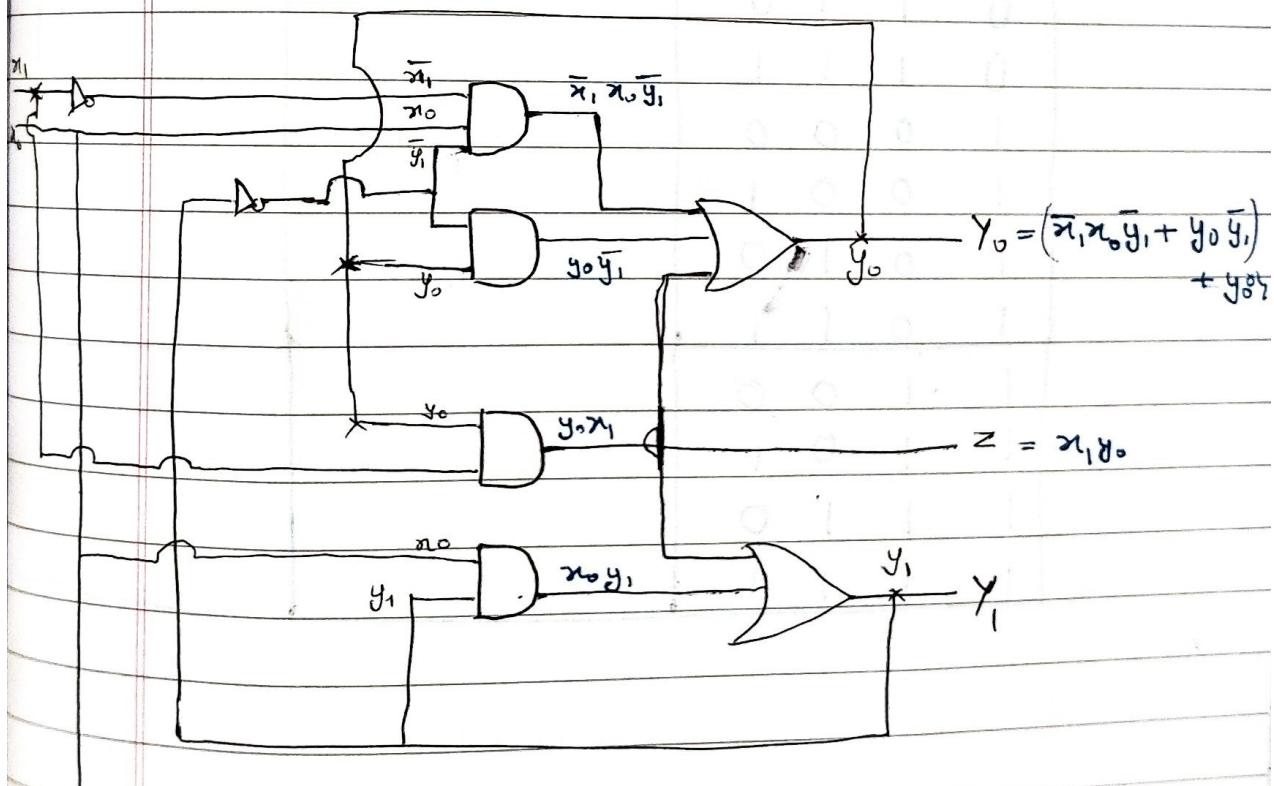Ques: for the following CKT find out present total states, next total states, stable state, O/p, transition table & flow table ?.




$$Y_0 = \bar{x}_1 x_0 \bar{y}_1 + y_0 \bar{y}_1 + y_0 \bar{x}_1$$

$$Y_1 = y_0 \bar{x}_1 + x_0 y_1$$

$$Z = x_1 y_0$$

## # Asynchronous Sequential CKT design

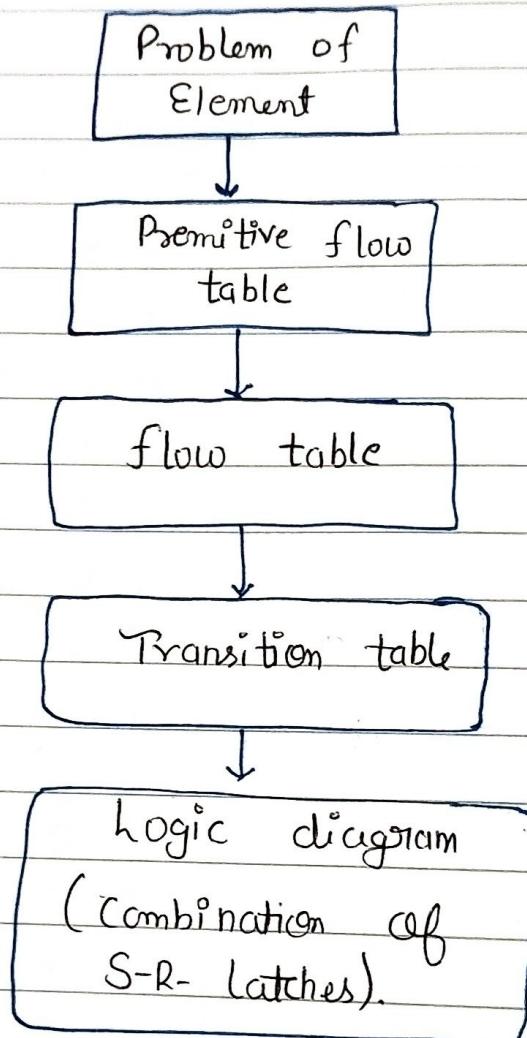

Ques:- Design asynchronous S.C in gated latch with two i/p A&B and output Q. When B is 1, A is transferred to Q when B is 0, output remains in same state even if A changes its value?

Ans.

$$B = 1, Q = A$$

$$B = 0, Q = \text{Prev. o/p}$$


State	A	B	$\varphi$
a	0	1	0
b	0	0	0
c	1	0	0
d	1	1	1
e	1	0	1
f	0	0	1

» Primitive flow table



	AB	00	01	11	10	
a	b,-	(@,0	d,-	-,-	-	}
b	(0)	a,-	--,-	c,-	-	}
c	b,-	--,-	d,-	(0,0	-	}
d	--,-	a,-	(0,1	e,-	-	}
e	f,-	--,-	d,-	(0,1	-	}
f	(0,1	a,-	--,-	e,-	-	




[stable state नहीं होता - ]

Fundamental mode

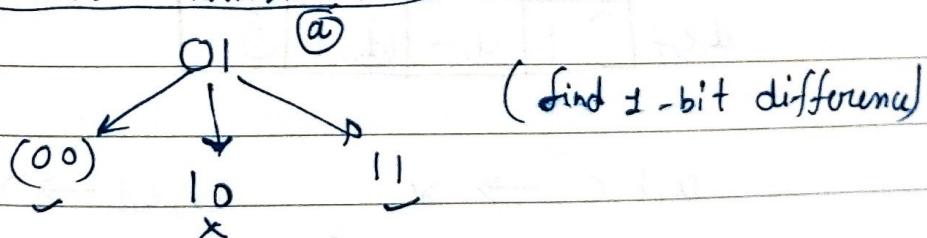

(b).

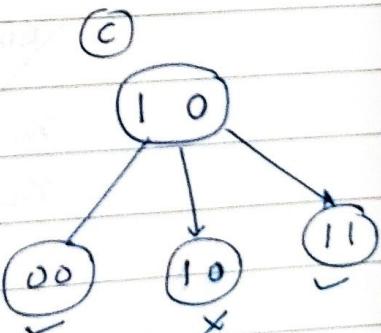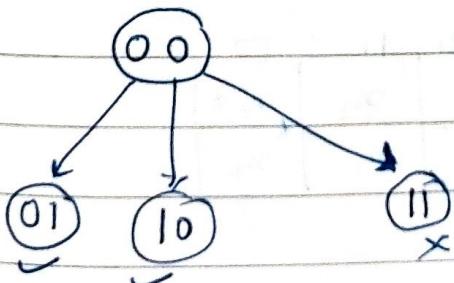

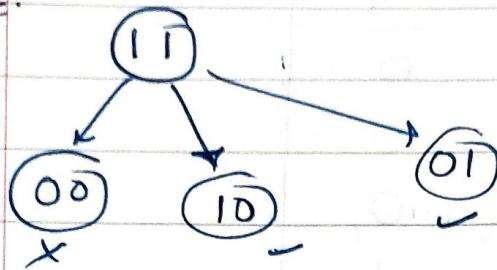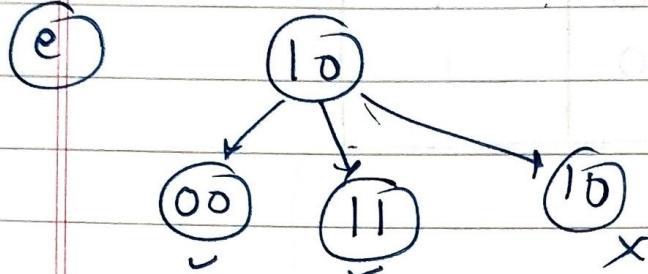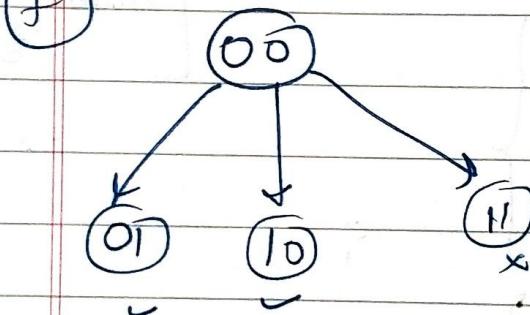d.e.f.» Reduce table

AB

	00	01	11	10
a, b, c	b, 0	a, 0	d, -	c, 0
d, e, f	d, 1	a, -	d, 1	c, 1

 $a, b, c \rightarrow x_1$  $d, e, f \rightarrow x_2$ 

AB


	00	01	11	10
$x_1$	$x_1$	$x_1$	$x_2$	$x_1$
$x_2$	$x_2$	$x_1$	$x_2$	$x_2$

» transition table


$$x_1 = 0 \rightarrow x_2 = 1 \quad (\text{left})$$

y	AB		00	01	11	10
	0	1	0	1	1	0
1	1	0	1	1	1	1

$$Y = AB + \bar{Y}B$$

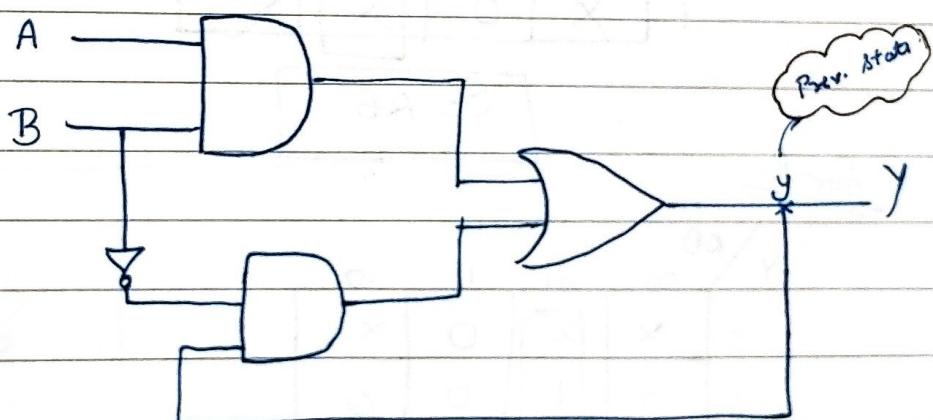» Ckt diagram

→ Asynchronous Sequential Ckt by S-R-latch  
 ↳ by using ~~NOR~~ NOR - Gate.

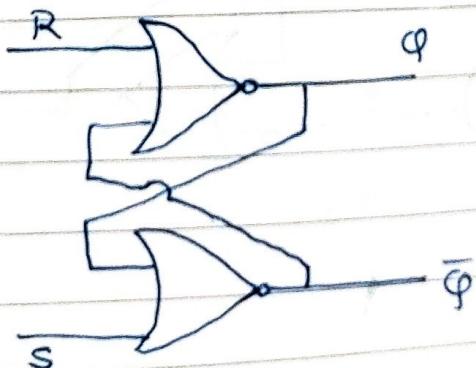S.R. Latch

Excitation table

P.S	N.S	S	R
0	0	0	X
0	1	1	0
0	0	0	1
0	1	X	0

AB \ Y

		00	01	11	10
0	00	0	0	1	0
	11	1	0	1	1
1	00	0	1	0	0

» K-map for S

AB \ Y

		00	01	11	10
0	00	0	0	1	0
	11	X	0	X	X
1	00	0	1	0	0


$$S = AB$$

for R,

AB \ Y

		00	01	11	10
0	00	X	X	0	X
	11	0	1	0	0
1	00	0	1	0	0

$$R = \bar{A}B$$

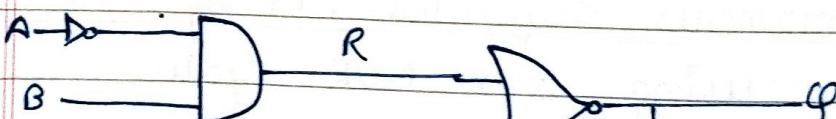Ckt.

2 or 5 Marks  
Imp.

classmate


Date \_\_\_\_\_  
Page \_\_\_\_\_

## # HAZARDS


» Hazards are unwanted switching transient that may appear at the o/p of a ckt because of different path exhibit different propagation delay.

» Types of Hazards -


(1) Static 1 (one) Hazard -

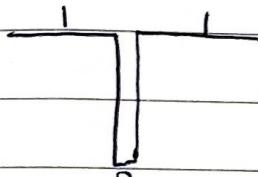

(2) Static '0' Hazard -

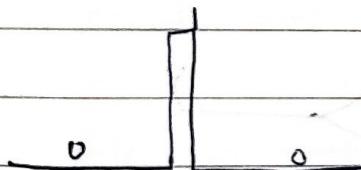


(3) Dynamic Hazard

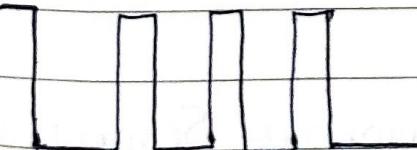

(4) Essential Hazard -

Eg.

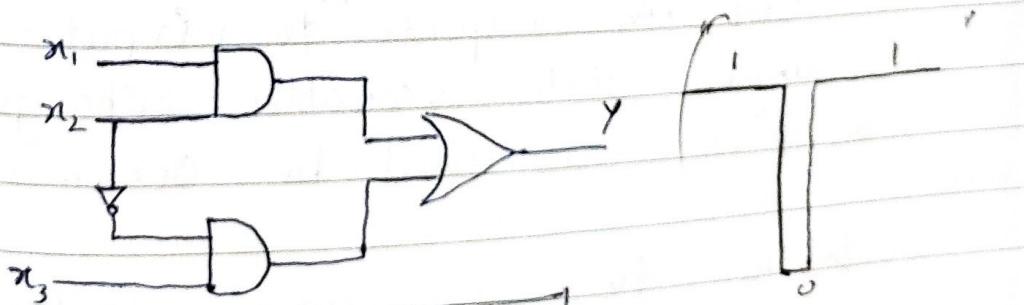

$$Y = x_1 x_2 + \bar{x}_2 x_3$$


usingInverse K-map

$x_1 \backslash x_2, x_3$	00	01	11	10
0	1	1		
1	1	1	1	1

we add this group for remove (Hazard)

$$Y = x_1 x_2 + \bar{x}_2 x_3 + x_1 x_3 \quad \text{(Hazard free eqn)}$$

now,

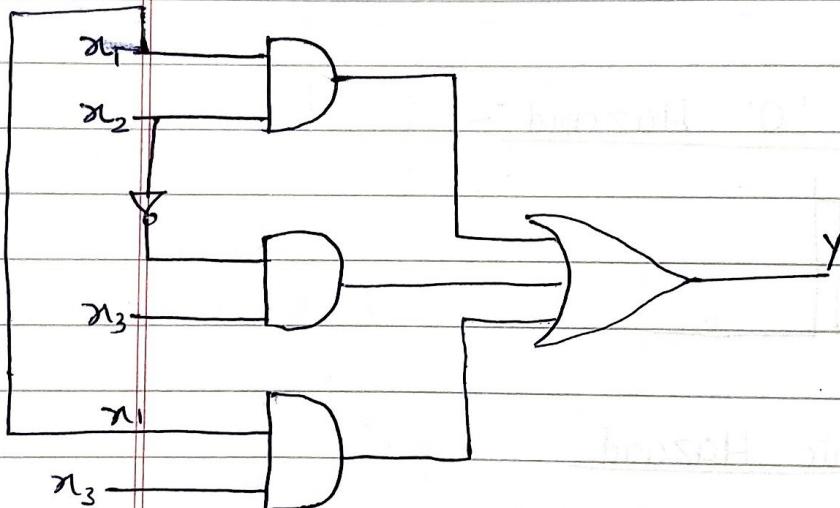CKT diagram

## # Races in Asynchronous Sequential CKT

» When input is applied to asynchronous CKT in response to input two or more state variables change simultaneously then race will be occur.

» When two or more feedback variables

changes value in response to a change in input variable with unequal propagation delay than a race condition exists in an asynchronous sequential ckt.

### Eq: Transition table

$y_1, y_2$	$x$	0	1
00	11	00	(00)
01	00	11	
11	00	(11)	
10	00	11	

→ 2 bit difference

00 → 11 → race cond<sup>n</sup>

01 → 00 → (x)

01 → 11 → (x)

11 → 00 → ✓      (race cond<sup>n</sup> exists)

### # Types of race condition

(1) Critical race      (2) Non-critical race

#### \* Critical race -



- If there is a race in a circuit and ckt reaches in different final, final stable state depending upon the order of change of state variable then race is called "critical race".

- Critical race may always go to some wrong state
- It is due to different propagation delay.
- Identical CKT with different propagation delay may go to different wrong state.

Eg. Transition table

$y_1 y_2 \backslash x$	0	1
00	11	(00)
01	(01)	00
11	(11)	01
10	(10)	00

race condition exists

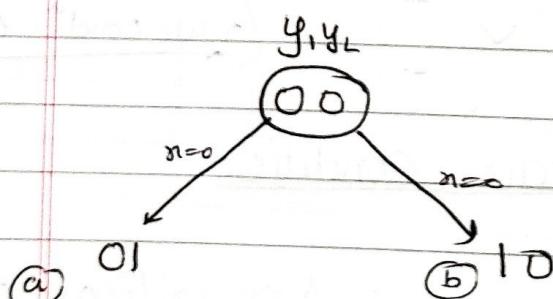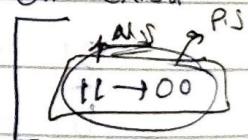

$$a) 00 \xrightarrow{x=0} 01 \xrightarrow{x=0} (01) \text{ (stable state)}$$


$$b) 00 \xrightarrow{x=0} 10 \xrightarrow{x=0} (10) \text{ (stable state)}$$

★ In all transitions final stable states are different, so the race is critical.




\* non-critical race -

- The final stable state will be same in non-critical race.
- In non-critical race may always go to the correct final state after its transition through unstable states.
- It is also due to different propagation delay.

Eg: Transition table

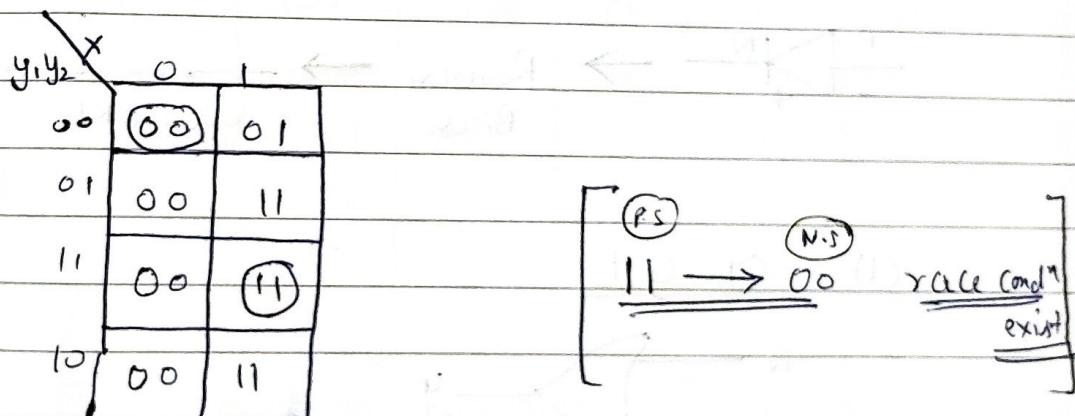

$y_1, y_2$

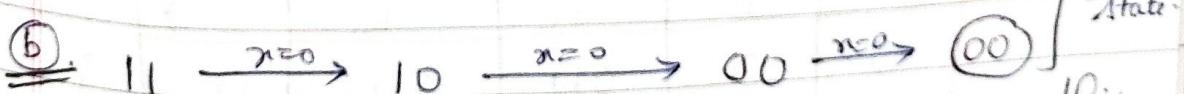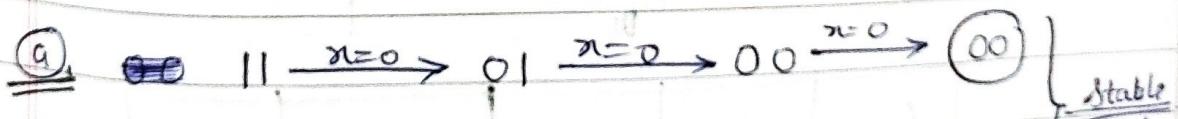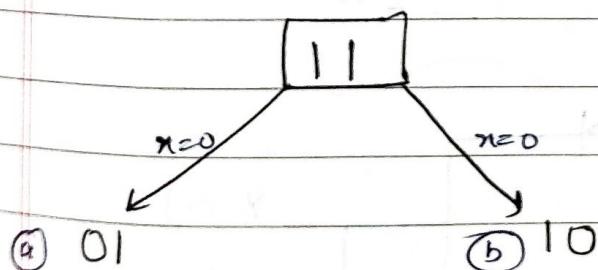

Hence, both states are same so, this is non-critical race cond'.